

VE311 FINAL RC - Single Stage Amplifier

Runxi Wang

UM-SJTU JI

wangrunxi@sjtu.edu.cn

December 9, 2021

Overview

Basics

DC

g_m & r_o & g_{mb}

G_m & R_{out} & R_{in} & A_v

Circuits and Formulas

Common Source

Source Degradation

Source Follower

Common Gate

Tips



DC Calculation

Current (NMOS)

Non-saturation region:

$$I_D = \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Saturation region:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

where $V_{TH} = V_{TO}$, $\frac{W}{L_{eff}} = \frac{W_{drawn}}{L_{drawn} - 2LD}$, $C_{ox} = \frac{\epsilon_r \epsilon_0}{TOX}$, and $\mu_n = UO \times 10^{-4}$

gm & r_o & gmb

For NMOS,

$$gm = \frac{\partial I_D}{\partial V_{GS}} = \frac{2I_D}{V_{GS} - V_{TH}}$$

$$r_o = \frac{\partial V_{DS}}{\partial I_D} \approx \frac{1}{I_D \lambda}$$

$$gmb = \frac{\partial I_D}{\partial V_{SB}} = -\mu_n C_{ox} \frac{W}{L_{eff}} (V_{GS} - V_{TH}) \cdot \frac{\gamma}{2} \cdot \frac{1}{\sqrt{|2\phi_F + V_{SB}|}}$$

where $\lambda = LAMBDA$, $\gamma = GAMMA$, and $2\phi_F = PHI$.

G_m & R_{out}

How to calculate G_m ?

1. Draw small signal model.
2. Connect port with V_{out} to ground.
3. Derive i_{out} .
4. Calculate $G_m = \frac{i_{out}}{V_{in}}$.

How to calculate R_{out} ?

1. Draw small signal model.
2. Connect port with V_{in} to ground. Connect a test voltage v_t on port with V_{out} .
3. Derive i_t .
4. Calculate $R_{out} = \frac{v_t}{i_t}$.

$R_{in} \text{ \& } A_v$ **How to calculate R_{in} ?**


1. Draw small signal model.
2. Connect port with V_{out} to ground. Connect a test voltage v_t on port with V_{in} .
3. Derive i_t .
4. Calculate $R_{in} = \frac{v_t}{i_t}$.

How to calculate A_v ?

$$A_v = GmR_{out}$$

Common Source with Resistive Load

Basic Circuit ($\lambda, \gamma \neq 0$)

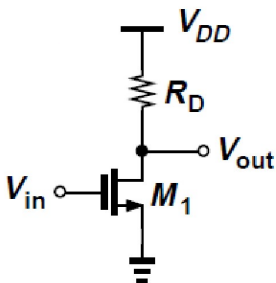

$$G_m = -g_{m1}$$


$$R_{out} = r_o \parallel R_D$$

$$A_v = -g_{m1}(r_o \parallel R_D)$$

- * What if R_D is replaced by a DC current source? (slide page 9)
- * What if M_1 is a PMOS?

Common Source with Diode-Connected Load

Basic Circuit ($\lambda, \gamma \neq 0$)

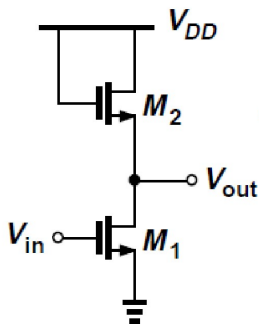

$$\Rightarrow \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2}$$



$$Gm = -gm_1$$

$$R_{out} = r_{o1} \parallel \frac{1}{g_{m2}} \parallel \frac{1}{g_{mb2}} \parallel r_{o2}$$

$$A_v = -gm_1 \left(r_{o1} \parallel \frac{1}{gm_2} \parallel \frac{1}{gmb_2} \parallel r_{o2} \right)$$

Common Source with Diode-Connected Load (Cont.)

Basic Circuit ($\lambda, \gamma \neq 0$)

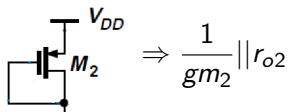
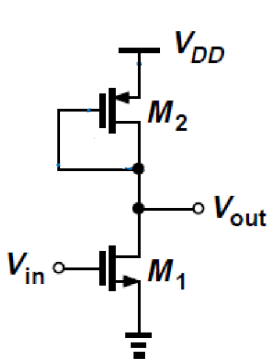


$$G_m = -gm_1$$

$$R_{out} = r_{o1} \parallel \frac{1}{gm_2} \parallel r_{o2}$$

$$A_v = -gm_1 \left(r_{o1} \parallel \frac{1}{gm_2} \parallel r_{o2} \right)$$

Basic Circuit ($\lambda, \gamma \neq 0$)

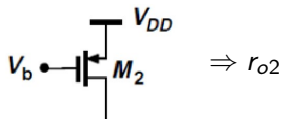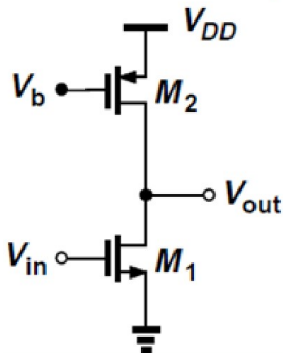


$$Gm = -gm_1$$

$$R_{out} = r_{o1} || r_{o2}$$

$$A_v = -gm_1 (r_{o1} || r_{o2})$$

Common Source with Source Degradation

Basic Circuit ($\lambda, \gamma \neq 0$)

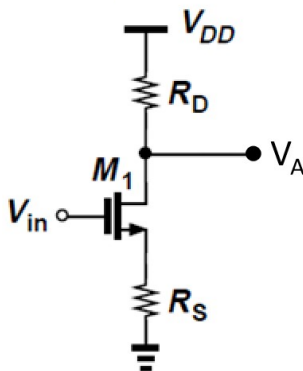


$$Gm = \frac{-gm_1 r_{o1}}{R_S + r_{o1} + (gm_1 + gmb_1) r_{o1} R_S}$$


$$R_{out} = [R_S + r_{o1} + (gm_1 + gmb_1) r_{o1} R_S] \parallel R_D$$

* What if M_1 is a PMOS?

Common Source with Source Degradation (Cont.)

Basic Circuit ($\lambda, \gamma \neq 0$)

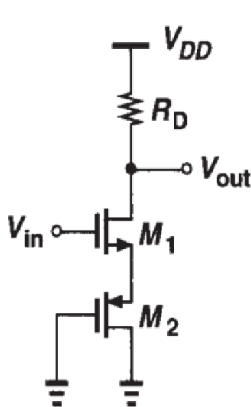



$$\Rightarrow \frac{1}{gm_2} \parallel \frac{1}{gmb_2} \parallel r_{o2}$$


$$Gm = \frac{-gm_1 r_{o1}}{R_S + r_{o1} + (gm_1 + gmb_1) r_{o1} R_S}$$

$$R_{out} = [R_S + r_{o1} + (gm_1 + gmb_1) r_{o1} R_S] \parallel R_D$$

with R_S replaced by $\frac{1}{gm_2} \parallel \frac{1}{gmb_2} \parallel r_{o2}$

Source Follower

Basic Circuit ($\lambda, \gamma \neq 0$)


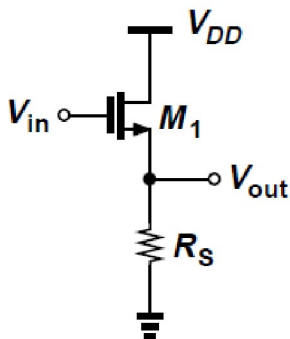


$$Gm = gm_1$$
$$R_{out} = r_{o1} || R_S || \left(\frac{1}{gm_1 + gmb_1} \right)$$

* What if M_1 is replaced by a PMOS?


Source Follower with Current Source

Basic Circuit ($\lambda, \gamma \neq 0$)

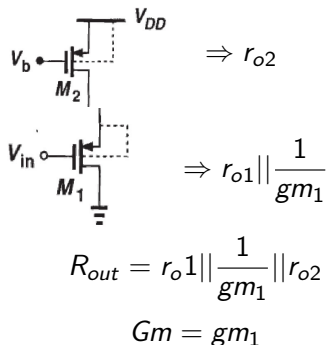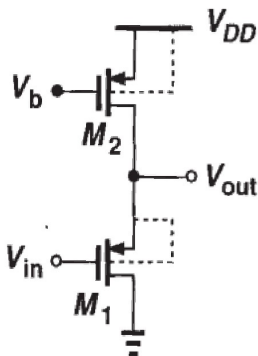

Common Gate

Basic Circuit ($\lambda, \gamma \neq 0$)

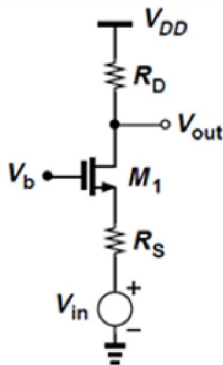

$$G_m = \frac{(g_{m1} + g_{mb1})r_{o1} + 1}{r_{o1} + R_S + (g_{m1} + g_{mb1})r_{o1}R_S}$$


$$R_{out} = R_D \parallel [r_{o1} + R_S + (g_{m1} + g_{mb1})r_{o1}R_S]$$


$$\Rightarrow \frac{R_D + r_{o1}}{1 + (g_{m1} + g_{mb1})r_{o1}}$$


* What if M_1 is replaced by PMOS?

Complex Common Gate

$$(\lambda, \gamma \neq 0)$$

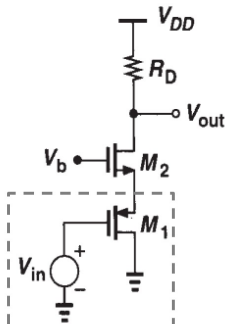

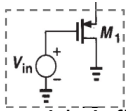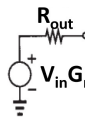For , take it as a source follower with infinity source resistance. Then we get



$$\left\{ \begin{array}{l} G_m = g_{m1} \\ R_{out} = r_{o1} \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{mb1}} \end{array} \right.$$

Some Tips qwq

- Derive all the G_m and R_{out} yourself before the final.
- Small signal model!!!
- Small signal models, equations, and explanation do matter if you cannot guarantee your final result is correct.
- When plotting, please mark your diagram well!!!(peak values, period. . .).

Good Luck for Your FINAL!

